AN10923

AMPLEON

1.5 GHz Doherty power amplifier for base station applications using the BLF6G15L-250PBRN

Rev. 2 — 1 September 2015

Application note

Document information

Info	Content	
Keywords	RF power transistor, Doherty architecture, LDMOS, Power amplifier, W-CDMA, LTE, Base station, BLF6G15L-250PBRN	
Abstract	This application note describes the design and performance of a power amplifier for 1.5GHz 3GPP E-UTRA LTE base stations using two BLF6G15L-250PBRN LDMOS power transistors in Doherty architecture	

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

Revision history

Rev	Date	Description
AN10923#2	20150901	Modifications
		The format of this document has been redesigned to comply with the new identity guidelines of Ampleon.
		Legal texts have been adapted to the new company name where appropriate.
AN10923#1	20110314	Initial version

Contact information

For more information, please visit: http://www.ampleon.com

For sales office addresses, please visit: http://www.ampleon.com/sales

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

1. Introduction

This application note describes the design and performance of a Doherty power amplifier optimized for use in 1.5 GHz 3GPP E-UTRA LTE base stations applications. The amplifier design, characteristics and the test methods used to determine the RF performance are also described.


The amplifier uses two BLF6G15L-250PBRN LDMOS power transistors in a Doherty architecture. The design ensures high efficiency while providing a peak power capability very similar to two parallel Class AB amplifiers. The input and output sections are internally matched, giving high gain with good gain flatness and phase linearity over a wide frequency band.

The BLF6G15L-250PBRN transistor is a sixth generation device using Ampleons' advanced LDMOS process.

2. Circuit description

The 1.5 GHz Doherty power amplifier employing two BLF6G15L-250PBRN power transistors is shown in the photograph of Figure 1. The main amplifier is biased to operate in Class-AB mode and the peak amplifier is biased to operate in Class-C mode. The input signal is split by a 3 dB power divider and fed to each amplifier with a 90 degree phase difference. The amplified signals are recombined at the output with a power combiner. Both amplifiers operate when the input signal peaks, and each is presented with the load impedance that enables maximum output power. If the input signal amplitude drops below a preset threshold level, the Class-C peaking amplifier turns off and only the Class-AB remains active. At these lower power levels the Class-AB main amplifier is presented with higher load impedance that enables higher efficiency and gain. The result is an extremely efficient solution for amplifying the complex modulation schemes employed in current and emerging wireless systems.

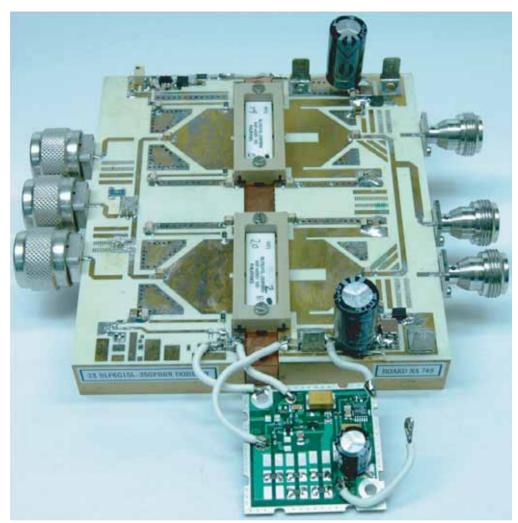1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN



019aab216

Fig 1. Photograph of the BLF6G15L-250PBRN Doherty power amplifier

3. Design and Tuning

The two-way symmetrical Doherty amplifier comprising a main amplifier and a peak amplifier, input phase splitter and power combiner was designed and optimized using the following target specification:

- Frequency band 1476 MHz to 1511 MHz
- 2-carrier W-CDMA 3 GPP, 64 DPCH, PAR = 7.5 dB at 0.01% probability per carrier, 5 MHz carrier spacing
- Drain-source voltage (V_{DS}) = 32 V
- P_{L(3db)} = 58 dBm
- P_{L(AV)} = 49 dBm
- Linear gain = 15 dB

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

- Gain ripple 0.5 dB
- RLin 15 dB
- ACPR at 5 MHz offset and P_{L(AV)} = −30 dBc
- Efficiency at P_{L(AV)} = 36 %
- PCB material RO4350 30 mils

The description of the design of the single stage (Class-AB) amplifier is given in <u>Section 3.1</u>, and the description of the Doherty design is given in <u>Section 3.2</u>.


3.1 Design of the single stage amplifiers

The design began with calculation of the input and output requirements of a single stage amplifier working in Class-AB matched to 50 Ω (main amplifier). Table 1 gives the typical source and load impedances used in the matching circuit of the single stage amplifier.

The peak amplifier uses the same input and output matching design as the main amplifier. The only difference between the two amplifiers is in the bias conditions. The main amplifier is biased in Class-AB with I_{Dq} current of 1450 mA while the peak amplifier is biased in Class-C with V_{GS} of 0.4V.

Table 1. Typical impedance per section

Frequency (GHz)	Z _S (Ω)	Z _L (Ω)
1.48	1.12 - j2.80	1.67 - j3.33
1.51	1.32 - j2.79	1.59 - j3.73

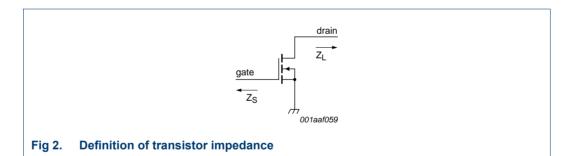

3.2 Doherty design

For Doherty operation, the output-matching network of the main amplifier should also have the property of an impedance inverter. In order to achieve this a 50 Ω stripline is added to the output matching circuit.

The peak amplifier in inactive mode has finite off-state impedance and will therefore absorb power from the main amplifier. This loss is minimized by inserting a 50 Ω stripline whose length is chosen for the maximum impedance at the combining point of the power combiner when the peak amplifier is in off-state.

In order to get maximum output power from the Doherty amplifier it is necessary to provide the correct input drive level and phase to the peak and main amplifiers. Because the main and the peak amplifiers have similar gains, a symmetrical 3 dB, 90 degrees phase difference hybrid coupler is used to split the signal at the input.

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

It is essential that the signals from the main and peak amplifiers arrive in phase at the combining point of the power combiner. The phase difference introduced by the length of impedance inverter stripline and the off-state maximum impedance stripline therefore needs to be compensated for at the input. The phase difference caused by the different classes of operation is very small and can be ignored.

The drain bias line is one of the strongest contributors to the memory effects by the amplifiers. Making the bias line as short as possible will have a positive effect on the memory performance. In order to further reduce the drain video impedance, two parallel bias lines are placed symmetrically on both sides of every transistor.

3.3 Tuning

Adjusting the bias of the peak amplifier can further optimize the back-off efficiency of the Doherty amplifier, however this will be at the cost of linearity. Another way to optimize linearity is by adjusting the input phase shift while monitoring the AM-AM and AM-PM characteristics. This however will be at the cost of peak power and peak efficiency.

3.4 Transistor biasing

There are two ways to bias the BLF6G15-250PBRN transistor. The first is standard bias without using the sense FETs integrated in the package. In this case the sense FET leads can be removed and the bias can be applied directly to the power transistor(s) (see Section 5 "Appendix A: PCB layout and bill of materials (no auto bias)". The second way of biasing is by using the sense leads. An auto bias circuit is required to provide a fixed I_{Dq} to the main RF FET. The FET is biased by a sense transistor mounted in the same package which is used as a current mirror. Details of the circuit and layout are given in Section 6 "Appendix B: PCB layout and bill of materials with auto bias", Figure 12 and Figure 13. The peak amplifier operates in Class-C and has a fixed gate-source voltage of 0.4 V.

4. Test results


4.1 Network analyzer frequency sweep

The network analyzer frequency sweep measurement results for the Doherty test board are shown in <u>Figure 3</u>. The test conditions were as follows:

- P_L= 49 dBm
- V_{DS} = 32 V
- I_{Dg} (main) = 1450 mA
- V_{GS} = 0.4 V (peak amplifier)

AN10923 **AMPLEON**

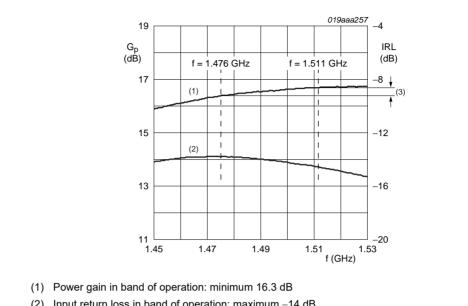1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN



- (2) Input return loss in band of operation: maximum -14 dB
- (3) Gain ripple in band of operation: maximum 0.3 dB

Power gain and input return loss as functions of frequency Fig 3.


4.2 Large signal power sweeps


4.2.1 CW network analyzer power sweep (AM-AM and AM-PM)

The network analyzer measurement results for the test board are shown in Figure 4 and Figure 5. The test conditions were as follows:

- V_{DS} = 32 V
- I_{Dq} (main) = 1450 mA
- V_{GS} = 0.4 V (peak amplifier)
- Network analyzer sweep time = 27.1 ms

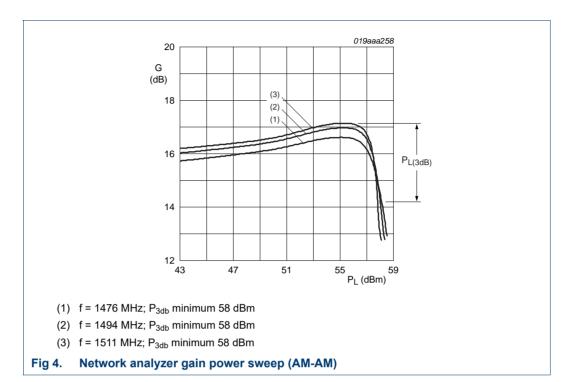1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN



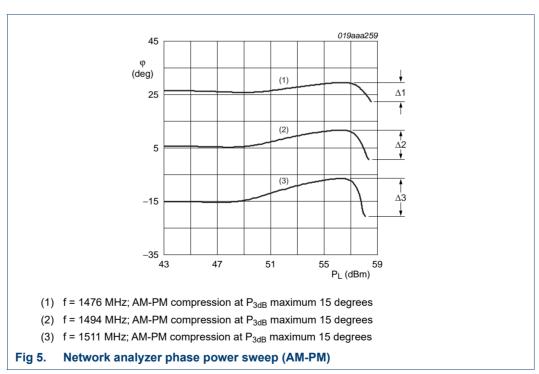


4.2.2 2-tone W-CDMA

The 2-carrier W-CDMA (5 MHz spacing) measurement results for the test board are shown in Figure 6 and Figure 7. The test conditions were as follows:

- V_{DS} = 32 V
- I_{Dq} (main) = 1450 mA

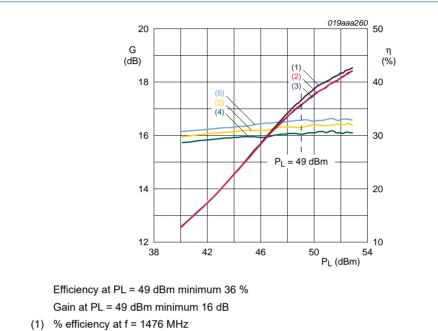
- V_{GS} = 0.4 V (peak amplifier)
- 3 GPP, Test Model 1, 64 DPCH, PAR = 7.5 dB at 0.01% probability per carrier, 5 MHz carrier spacing



- (2) % efficiency at f = 1494 MHz
- (3) % efficiency at f = 1511 MHz
- (4) dB gain at f = 1476 MHz
- (5) dB gain at f = 1494 MHz
- (6) dB gain at f = 1511 MHz

Fig 6. 2-carrier W-CDMA power sweep: gain as a function of output power

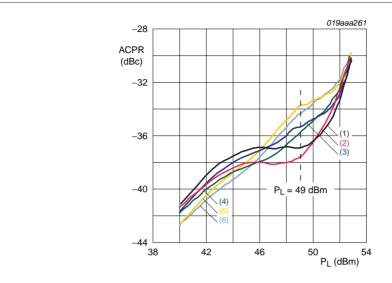1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN



ACPR at PL = 49 dBm minimum 34 dBc


- (1) 5 MHz, ACPR Hi, dBc at 1476 MHz
- (2) 5 MHz, ACPR Lo, dBc at 1476 MHz
- (3) 5 MHz, ACPR Hi, dBc at 1494 MHz
- (4) 5 MHz, ACPR Lo, dBc at 1494 MHz
- (5) 5 MHz, ACPR Hi, dBc at 1511 MHz
- (6) 5 MHz, ACPR Lo, dBc at 1511 MHz


Fig 7. 2-carrier W-CDMA power sweep: ACPR as a function of output power

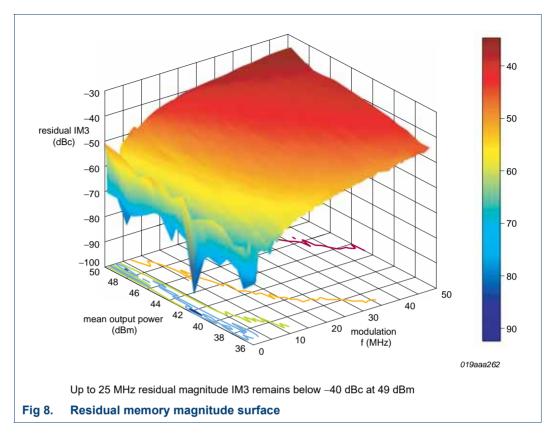4.3 Residual memory magnitude and phase surface plots large signal power sweeps

The residual memory surface versus tone spacing and mean output power measurement results for the test board are shown in <u>Figure 8</u>. and <u>Figure 9</u>. The test conditions were as follows:

- V_{DS} = 32 V
- I_{Dq} (main) = 1450 mA
- V_{GS} = 0.4 V (peak amplifier)



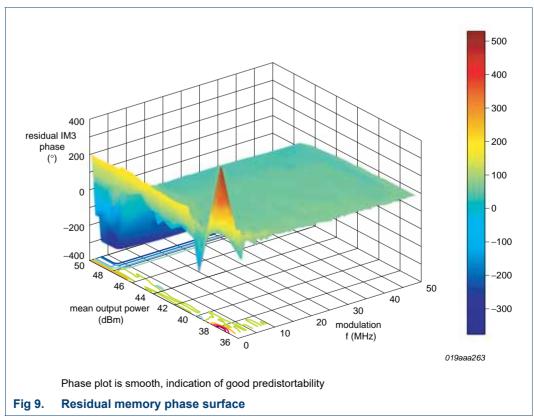

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

5. Appendix A: PCB layout and bill of materials (no auto bias)

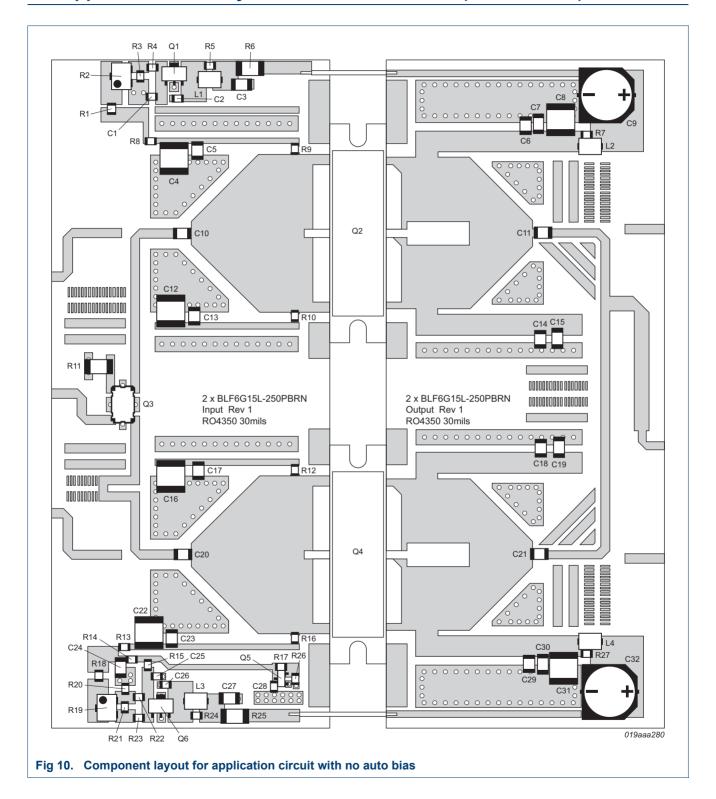


Table 2. Parts list for application circuit (no auto bias)

Component	Value	Description	Manufacturer
C1, C2, C25, C26	100 nF	capacitor	Murata GRM21BR71H104KA01L
C3, C24, C27, C28	1 μF	capacitor	Murata GRM31MR71H105KA88L
C4, C8, C12, C16, C22, C31	10 μF; 50 V	capacitor	Murata GRM32ER71H106KA12L
C5, C6, C10, C11, C13, C14, C17, C18, C20, C21, C23, C29	27 pF	capacitor, ATC 100B	American Technical Ceramics
C7, C15, C19, C30	470 nF; 50 V	ceramic capacitor	
C9, C32	470 μF; 63 V	electrolytic capacitor	
Q1, Q6	Regulator	JRC 78L08	
Q5	NPN transistor	PMBT2222	NXP Semiconductors
Q3	15 mm × 13 mm	3 dB hybrid XC1400P-03S	Anaren
Q2, Q4	LDMOS	BLF6G15L-250PBRN	Ampleon
L1, L2, L3, L4	26 mm × 5 mm	inductor	
R1, R18	2 kΩ, 1%	resistor, 0805	
R2, R19	200 Ω	potentiometer	
R20	75 Ω, 1%	resistor, 0805	
R3, R4, R21, R23	430 Ω, 1%	resistor, 0805	
R15, R22	1.1 kΩ, 1%	resistor, 0805	
R14	11 kΩ, 1%	resistor, 0805	
R13	820 Ω, 1%	resistor, 0805	
R8	5.1 Ω, 1%	resistor, 0805	
R9, R10, R12, R16	10 Ω, 1%	resistor, 0805	
R5, R7, R24, R27	9.1 Ω, 1%	resistor, 0805	
R6, R25	499 Ω, 0.5W, 5%	resistor, 2010	
R17	5.1 kΩ	resistor, 0805	
R26	910 Ω	resistor, 0805	
R11	50 Ω	50 $Ω$ load	

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

6. Appendix B: PCB layout and bill of materials with auto bias


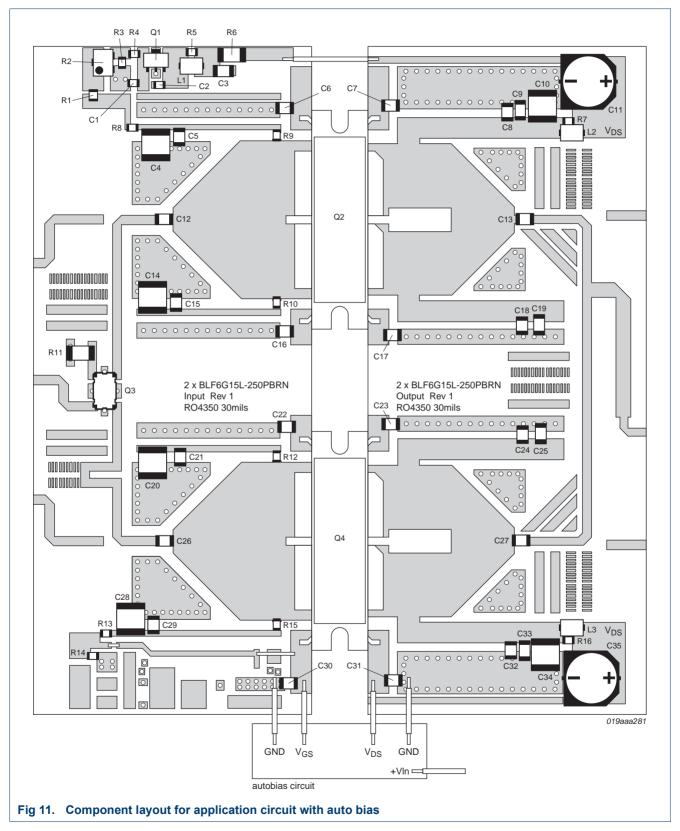


Table 3. Parts list for application circuit (auto bias)

Component	Value	Description	Manufacturer
C1, C2	100 nF	capacitor	Murata GRM21BR71H104KA01L
C3	1 μF	capacitor	Murata GRM31MR71H105KA88L
C4, C10, C14, C20, C28, C34	10 μF	capacitor	Murata GRM32ER71H106KA12L
C5, C6, C7, C8, C12, C13, C15, C16, C17, C18, C21, C22, C23, C24, C26, C27, C29, C30, C31, C32	27 pF	capacitor	
C9, C19, C25, C33	470 nF; 50 V	ceramic capacitor	
C11, C35	470 μF; 63 V	electrolytic capacitor	
Q1	regulator	JRC 78L08	
Q2, Q4	LDMOS	BLF6G15-250PBRN	Ampleon
Q3	15 mm × 13 mm	3 dB hybrid XC1400P-03S	Anaren
L1, L2, L3	26 mm × 5 mm	inductor	
R1, R14	2 kΩ, 1%	resistor, 0805	
R2	200 Ω	potentiometer	Bourns
R3, R4	430 Ω, 1%	resistor, 0805	
R5, R7, R16	9.1 Ω	resistor, 0805	
R6	499 Ω, 0.5 W, 5%	resistor, 2010	
R8	5.1 Ω, 1%	resistor, 0805	
R9, R10, R12, R15	10 Ω, 1%	resistor, 0805	
R11	50 Ω	50 $Ω$ load	
R13	820 Ω, 1%	resistor, 0805	

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

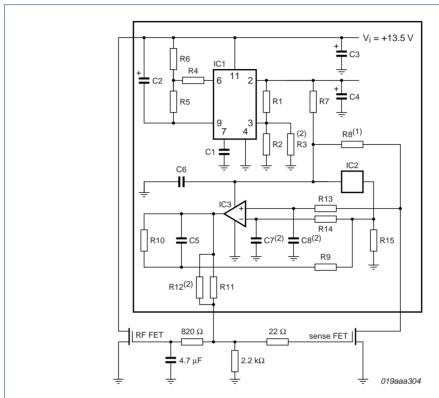7. Appendix C: Component layout auto bias board



- (1) R8 represents a batch of 1 to 9 resistors (a to j see Figure 13) which are used to set current.
- (2) Not mounted.

The components within the bounding frame are to be mounted on the auto bias board; all other components are to be mounted on the RF boards. Feed throughs are used to take the wires into the screened housing.

Fig 12. Circuit diagram of auto bias board

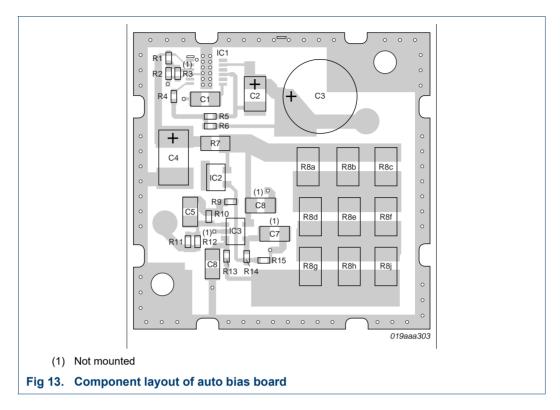


Table 4. Parts list for auto bias board

Component	Value	Description	Manufacturer
C1	1 nF	ceramic capacitor	
C2	2.2 μF	electrolytic capacitor	
C3	100 μF	electrolytic capacitor	
C4	10 μF	electrolytic capacitor	
C5	2.2 nF	ceramic capacitor	
C6	100 nF	ceramic capacitor	
IC1	-	LT3011	Linear Technology
IC2	-	LM4051	National Semiconductor
IC3	-	LM7341	National Semiconductor
R1, R6	1 ΜΩ	resistor, 0603	
R2, R3[1]	100 kΩ	resistor, 0603	
R4	4.7 kΩ	resistor, 0603	
R5	47 kΩ	resistor, 0603	
R7	4.7 Ω	resistor, 1206	
R8	57 Ω	up to 9 off; resistor, 0603	
R9	2.7 kΩ	resistor, 0603	
R10	56 kΩ	resistor, 0603	
R11, R12[1]	6.8 kΩ	resistor, 0603	
R13, R14, R15	10 kΩ	resistor, 0603	

^[1] Not mounted

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

8. Abbreviations

Table 5. Abbreviations

Acronym	Description
ACPR	Adjacent Channel Power Ratio
CCDF	Complementary Cumulative Distribution Function
CDMA	Code Division Multiple Access
EDGE	Enhanced Data rates for GSM Evolution
GSM	Global System for Mobile communication
IS-95	Interim Standard 95
LDMOS	Laterally Diffused Metal-Oxide Semiconductor
LDMOST	Laterally Diffused Metal-Oxide Semiconductor Transistor
PAR	Peak-to-Average power Ratio
RF	Radio Frequency
UMTS	Universal Mobile Telecommunications System
VSWR	Voltage Standing-Wave Ratio
W-CDMA	Wideband Code Division Multiple Access

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

9. Legal information

9.1 Definitions

Draft — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. Ampleon does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

9.2 Disclaimers

Limited warranty and liability — Information in this document is believed to be accurate and reliable. However, Ampleon does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information. Ampleon takes no responsibility for the content in this document if provided by an information source outside of Ampleon.

In no event shall Ampleon be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, Ampleon' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of Ampleon.

Right to make changes — Ampleon reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

Suitability for use — Ampleon products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an Ampleon product can reasonably be expected to result in personal injury, death or severe property or environmental damage. Ampleon and its suppliers accept no liability for inclusion and/or use of Ampleon products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

Applications — Applications that are described herein for any of these products are for illustrative purposes only. Ampleon makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using Ampleon products, and Ampleon accepts no liability for any assistance with applications or customer product design. It is customer's sole responsibility to determine whether the Ampleon product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

Ampleon does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using Ampleon products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). Ampleon does not accept any liability in this respect.

Export control — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

9.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own Any reference or use of any 'NXP' trademark in this document or in or on the surface of Ampleon products does not result in any claim, liability or entitlement vis-à-vis the owner of this trademark. Ampleon is no longer part of the NXP group of companies and any reference to or use of the 'NXP' trademarks will be replaced by reference to or use of Ampleon's own trademarks.

1.5 GHz Doherty power amplifier using the BLF6G15L-250PBRN

10. Contents

1	Introduction 3
2	Circuit description 3
3	Design and Tuning 4
3.1	Design of the single stage amplifiers 5
3.2	Doherty design
3.3	Tuning
3.4	Transistor biasing 6
4	Test results 6
4.1	Network analyzer frequency sweep 6
4.2	Large signal power sweeps 7
4.2.1	CW network analyzer power sweep (AM-AM and AM-PM)
4.2.2	2-tone W-CDMA 8
4.3	Residual memory magnitude and phase surface
	plots large signal power sweeps 10
5	Appendix A: PCB layout and bill of materials
	(no auto bias)
6	Appendix B: PCB layout and bill of materials with auto bias14
7	Appendix C: Component layout auto bias
	board
8	Abbreviations
9	Legal information
9.1	Definitions
9.2	Disclaimers
9.3	Trademarks19
10	Contents

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© Ampleon The Netherlands B.V. 2015. All rights reserved.

For more information, please visit: http://www.ampleon.com For sales office addresses, please visit: http://www.ampleon.com/sales